
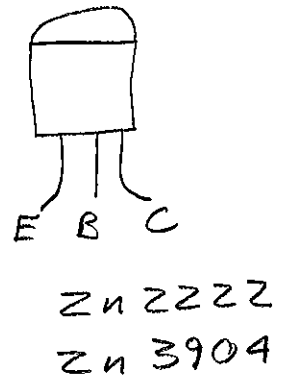


Inverting COR and PL Signals

- Using NPN transistor

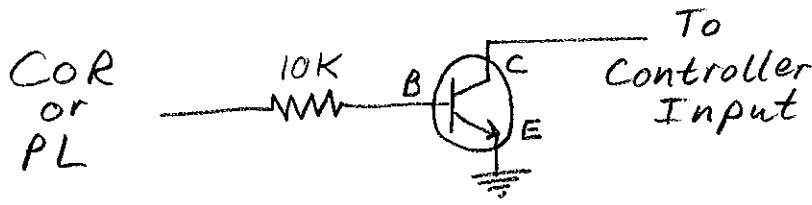

- Using Mosfet. This will work even with very weak signals.

