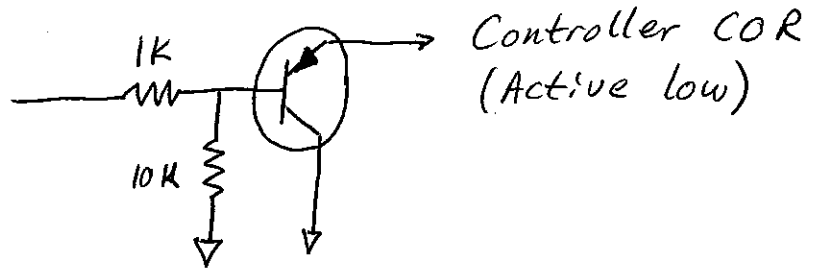


# Micor COR Buffer Circuit

8V (squelch closed)  
open (squelch open)



Use small-signal PNP transistor, such as a 2n3906.

