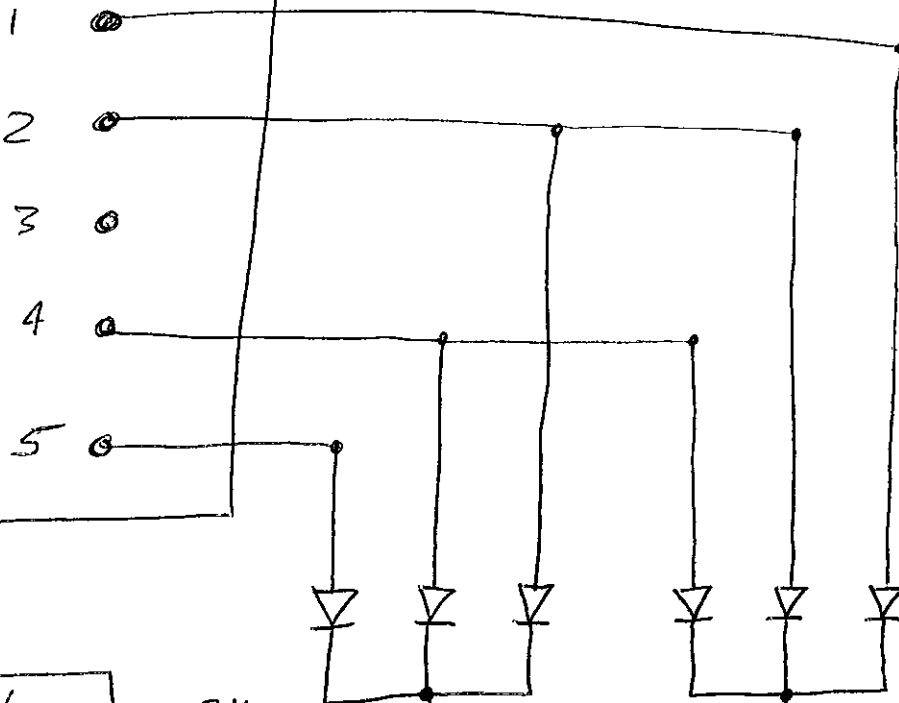


Selecting PL Frequencies

- Controller Output 1 pulls PL switch points 2, 4 and 5 low.
- Controller Output 2 pulls PL switch points 1, 2 and 4 low.

PL Select Switch



Controller Outputs

1

2

12V
↑
1KΩ

12V
↑
1KΩ