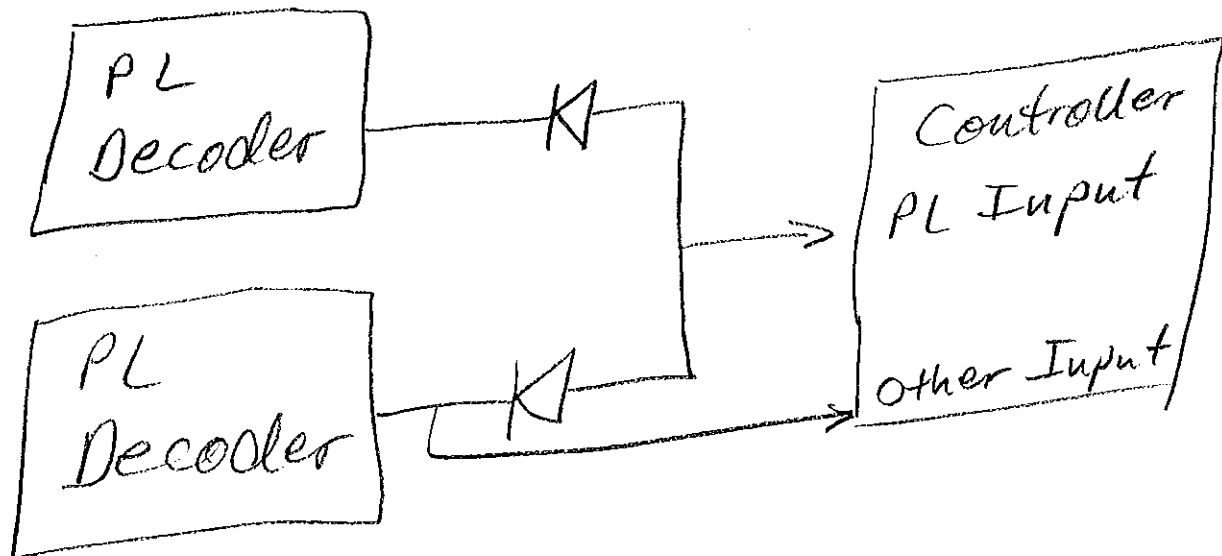


Using Two PL Tones

- One keys repeater only
- One also activates link



PL outputs must be active low (low when PL detected)